

**■ EFY LAB**

The diagram illustrates a complete IR remote control circuit. At its core is a yellow square IC1, labeled CD4047, which serves as a free-running multivibrator. The IC is connected to a 9V battery (BATT.) with its VDD pin (14) and GND pin (7) connected to the positive and negative rails, respectively. The output of the oscillator is taken from pin 10 (T1, BC547) and pin 12 (T2, BC557), which drive two LEDs (IR1, IR2, IR3) through a common resistor R4 (10K, 0.5W). The circuit is controlled by a push-to-on switch (S1) connected to pin 5 (DATA) through a 10K resistor (R2). A timing network consisting of a 10K resistor (R1) and a 390P capacitor (C1) is connected to pins 2 and 3. A second timing network with a 10K resistor (R3) and a 100μF capacitor (C2) is connected to pins 1 and 3. The circuit is powered by a 9V battery (BATT.) connected to the positive rail, and a 9V ON/OFF switch (S2) is connected to the negative rail.

Diagram showing the front view of two transistors:

- BC547 OR BC557:** A 3-pin transistor with pins labeled 1, 2, 3 and corresponding labels C, B, E below them.
- BS 170:** A 3-pin transistor with pins labeled D, G, S and corresponding labels D, G, S below them.

Assemble the circuit on a general-purpose PCB. Use switch S2 for power 'on'/'off' control. Commercially available IR receiver modules (e.g., TSOP1738) could be used for efficient reception of the transmitted IR signals. ●