## **SMART PHONE LIGHT**

The circuit shown here is used to switch on a lamp when the telephone rings, provided that the ambient light is insufficient. in the ambient light and greather than 100 kilo-ohms in darkness, is at the heart of the circuit.

The circuit is fully isolated from the

power failure or load shedding also.

The light switches off automatically after a programmable time period. If required, the lamp lighting period can





The circuit can be implemented using just two ICs. A light dependent resistance (LDR), with about 5 kilo-ohms resistance phone lines and it draws current only when the phone rings. The lamp can be battery powered to provide light during be extended by simply pressing a pushbutton switch (S1).

The first part of the circuit functions as a ring detector. When telephone is onhook, around 48V DC is present across the TIP and RING terminals. The diode in the opto-coupler is 'off' during this condition and it draws practically no current from the telephone lines. The optocoupler also isolates the circuit from the telephone lines. Transistor in the opto-coupler is normally 'off' and a voltage of +5V is present at the ring indicator line B.

When telephone rings, an AC voltage of around 70-80V AC present across the telephone lines turns on the diode inside the opto-coupler (IC2), which in turn switches on transistor inside the optocoupler. The voltage at its collector drops to a low level during ringing to trigger IC3 74LS123(A) monostable flip-flop.

The other opto-coupler (IC1) is used to detect the ambient light condition. When there is sufficient light, LDR has a low resistance of about 5 kilo-ohms and the transistor inside the opto-coupler is in 'on' state. When there is insufficient light available, the resistance of LDR increases to a few mega-ohms and the transistor switches to 'off' state. Thus the DC voltage present at the collector of transistor of the opto-coupler is normally low and it jumps to 5V when there is no light or insufficient light.

The 74LS123 retriggerable monostable multivibrator IC is used to generate a programmable pulse-width. The first monostable 74LS123(A) generates a pulse from the trigger input available during ringing, provided its pin 2 input (marked B) is logic high (i.e. during darkness). It remains high for the programmed duration and switches back to 0V at the end of the pulse period.

This high-to-low transition (trailing edge) is used to trigger the second monostable flip-flop 74LS123(B) in the same package. Output of the second monostable is used to control a relay. The lamp being controlled via the N/O contacts of the relay gets switched 'on.' The 'on' period can be extended by simply pressing pushbutton switch S1. If nobody attends the phone, the light turns off automatically after the specific time period equal to the pulse-width of the second flip-flop.

The light sensitivity of LDR can be changed by changing resistance R3 connected at collector of the transistor in light monitor circuit. Similarly, switch-on period of the lamp can be controlled by changing capacitor C3's value in the second 74123(B) monostable circuit.