

## SIDDHARTH SINGH AND SRINIVAS REDDY PINGLE

It is therefore necessary for all concerned to monitor the charge level of

Input from the battery under test is applied to LM3914 IC. This applied voltage is ranked anywhere between 0 and 10, depending upon its magnitude. The lower reference voltage of 10.1V is ranked

Another simple combinational logic



circuit can also be designed that will sound the buzzer when the display shows 9. Further charging should be stopped at this point in order to prevent overcharge.

The circuit is powered by the battery under test, via a voltage regulator IC. The circuit takes about 100 mA for its operation.

For calibrating the upper and lower reference levels, a digital multimeter

and a variable regulated power supply source are required. For calibrating the lower reference voltage, follow the steps given below:

- Set the output of power supply source to 10.1V.
- Connect the power supply source in place of the battery.
- Now the display will show some reading. At this point vary preset VR2 until the reading on the display just

changes from 1 to 0.

The higher reference voltage is calibrated similarly by setting the power supply to 13.8V and varying preset VR1 until reading on the display just changes from 8 to 9.

After the calibration is completed, the circuit may be housed in a suitable enclosure. The cost of all the components, including the enclosure, would be around Rs 200.